

Percobaan 1. Gerbang AND

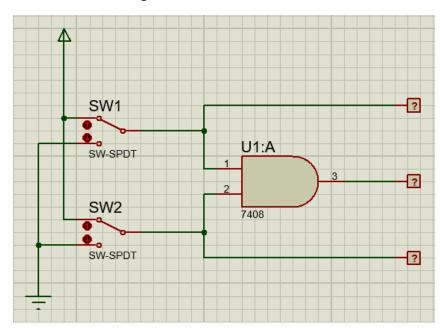


Tabel kebenaran

SW 1	SW 2	L1	L2	L3
0	0	0	0	0
1	0	1	0	0
0	1	0	1	0
1	1	1	1	1

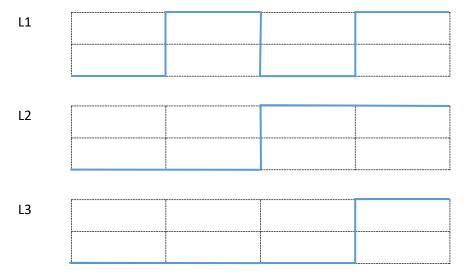


Percobaan 2. Gerbang OR

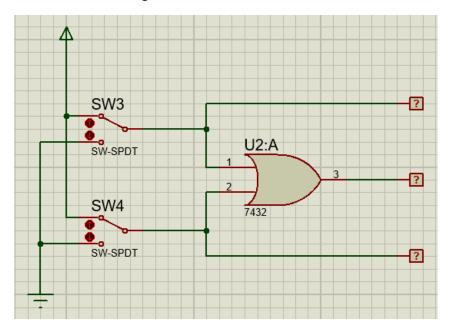


Tabel kebenaran

SW 1	SW 2	L1	L2	L3
0	0	0	0	0
1	0	1	0	1
0	1	0	1	1
1	1	1	1	1

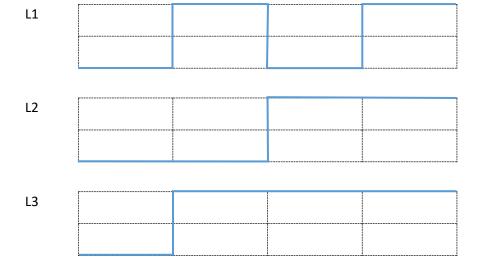

Percobaan 3. Gerbang NOT

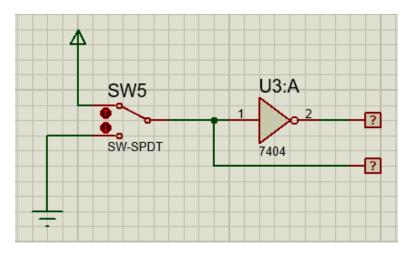


Tabel kebenaran

SW 1	L2	L1
0	0	1
1	1	0






Percobaan 4. Gerbang NAND

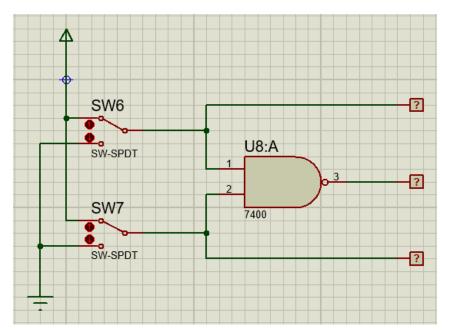


Tabel kebenaran

SW 1	SW 2	L1	L2	L3
0	0	0	0	1
1	0	1	0	1
0	1	0	1	1
1	1	1	1	0

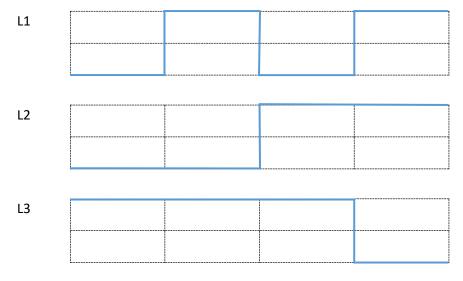


Percobaan 5. Gerbang NOR

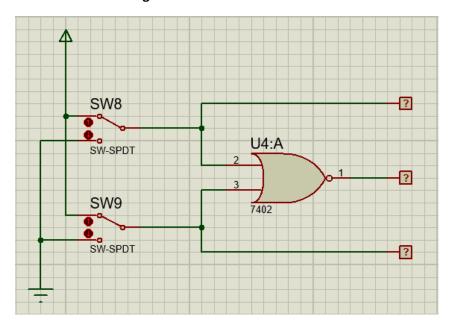


Tabel kebenaran

SW 1	SW 2	L1	L2	L3
0	0	0	0	1
1	0	1	0	0
0	1	0	1	0
1	1	1	1	0

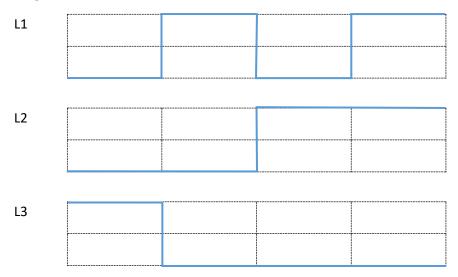


Percobaan 6. Gerbang XOR

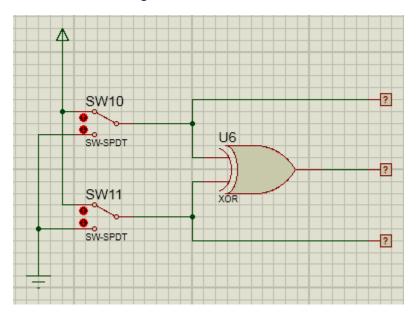


Tabel kebenaran

SW 1	SW 2	L1	L2	L3
0	0	0	0	0
1	0	1	0	1
0	1	0	1	1
1	1	1	1	0

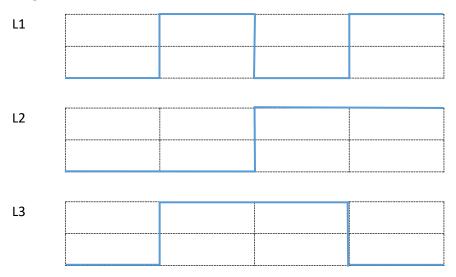

Percobaan 7. Gerbang XNOR

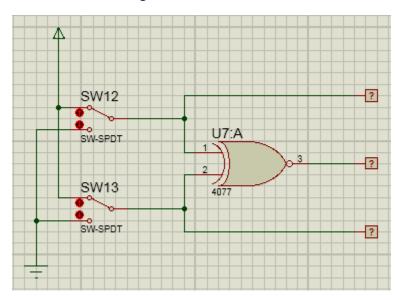

Tabel kebenaran

SW 1	SW 2	L1	L2	L3
0	0	0	0	1
1	0	1	0	0
0	1	0	1	0
1	1	1	1	1

